

Computer Architecture Laboratory

1st Experiment: 3-Digit BCD Adder

Name	Student #
Amirreza Aranpour	99170348
Ali Safarafard	99105583
Soroush Sherafat	99105504
Mehrad Milanloo	99105775

Design

Validating Input

At first, we know that if a digit of any of inputs is greater than 9, then the input is not a valid BCD number. So we design a `INPUT_VALIDATOR` subcircuit which generates an `IS_INPUT_VALID` output bit.

To implement this subcircuit we need to implement a `IS_GT9` subcircuit first. This subcircuit must return a single bit, showing whether a 5-bit input is greater than 9 or not. Here's the truth table:

Number	a_4	a_3	a_2	a_1	a_0	out
0	0	0	0	0	0	0
1	0	0	0	0	0	0
2	0	0	0	1	0	0
3	0	0	0	1	0	0
4	0	0	1	0	0	0
5	0	0	1	0	0	0
6	0	0	1	1	0	0
7	0	0	1	1	0	0
8	0	1	0	0	0	0
9	0	1	0	0	0	0
10	0	1	0	1	0	1
11	0	1	0	1	0	1
12	0	1	1	0	0	1
13	0	1	1	0	0	1
14	0	1	1	1	0	1
15	0	1	1	1	0	1
16	1	0	0	0	0	1
17	1	0	0	0	0	1
18	1	0	0	1	0	1
19	1	0	0	1	0	1
20	1	0	1	0	0	1

Number	a_4	a_3	a_2	a_1	a_0	out
21	1	0	1	0	0	1
22	1	0	1	1	0	1
23	1	0	1	1	0	1
24	1	1	0	0	0	1
25	1	1	0	0	0	1
26	1	1	0	1	0	1
27	1	1	0	1	0	1
28	1	1	1	0	0	1
29	1	1	1	0	0	1
30	1	1	1	1	0	1
31	1	1	1	1	0	1

Here's the equation:

$$out := a_4 \vee (a_3 \wedge a_2) \vee (a_3 \wedge a_1)$$

Adding

We realize that just like binary adders, n-digit BCD adders are composed of n 1-digit BCD adders with connected *Cins* and *Couts* and therefore, we need to design 1-digit BCD adders.

A 1-digit BCD adder is a 4-bit binary adder under the hood, with one difference: if the sum is greater than 9, we will output $Sum - 10$ as *Sum* and 1 as *Cout*. We reuse the **IS_GT9** subcircuit to detect these cases.

To generate $Sum - 10$, we use another 4-bit binary adder. Here is its second operand's truth table:

$gt9$	out_3	out_2	out_1	out_0
0	0	0	0	0
1	0	1	1	0

So we get the following equations:

$$out_3 := 0, out_2 := gt9, out_1 := gt9, out_0 := 0$$

To design a 4-bit binary adder, we need full adders and to design full adders, we need half adders.

Modules

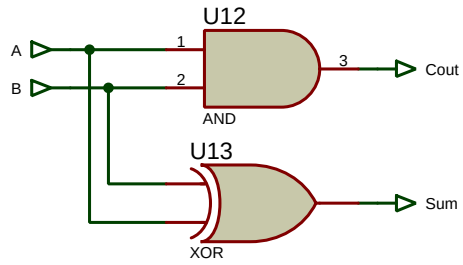


Figure 1: HA module.

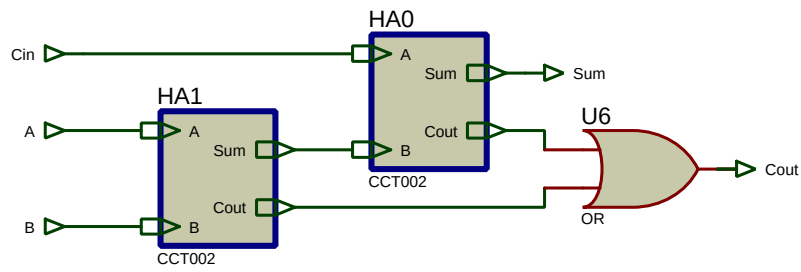


Figure 2: FA module.

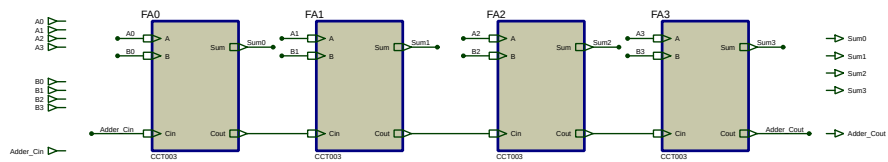


Figure 3: 4BIT_ADDER module.

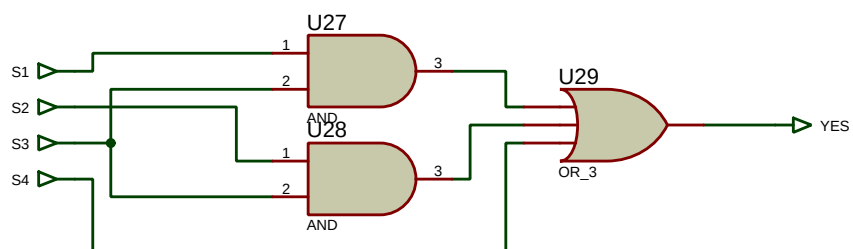


Figure 4: IS_GT9 module.

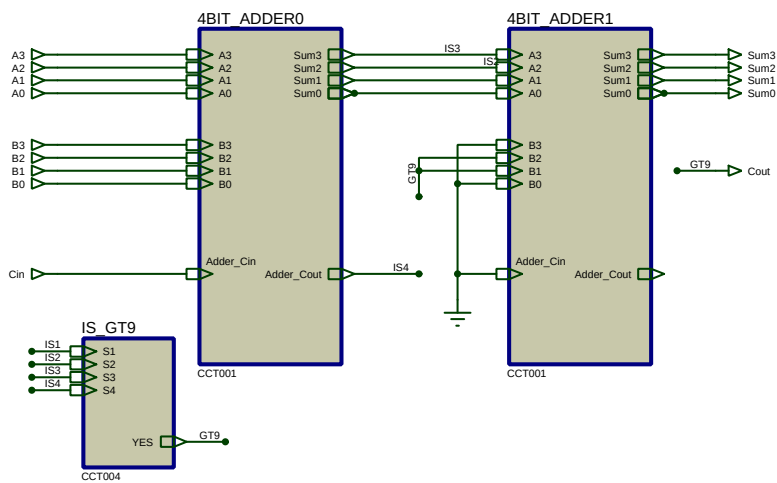


Figure 5: 1DIGIT_BCD_ADDER module.

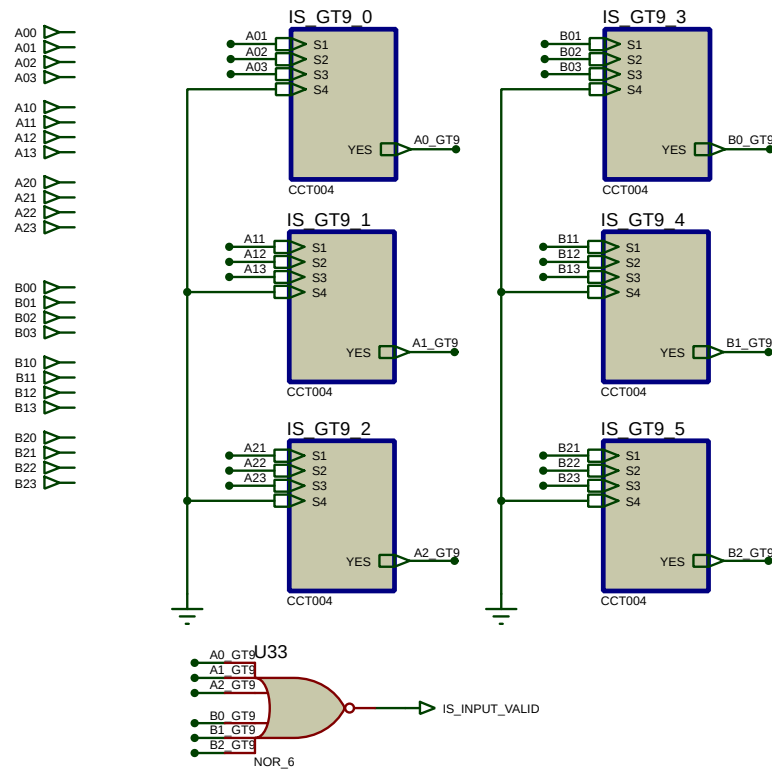


Figure 6: INPUT_VALIDATOR module.

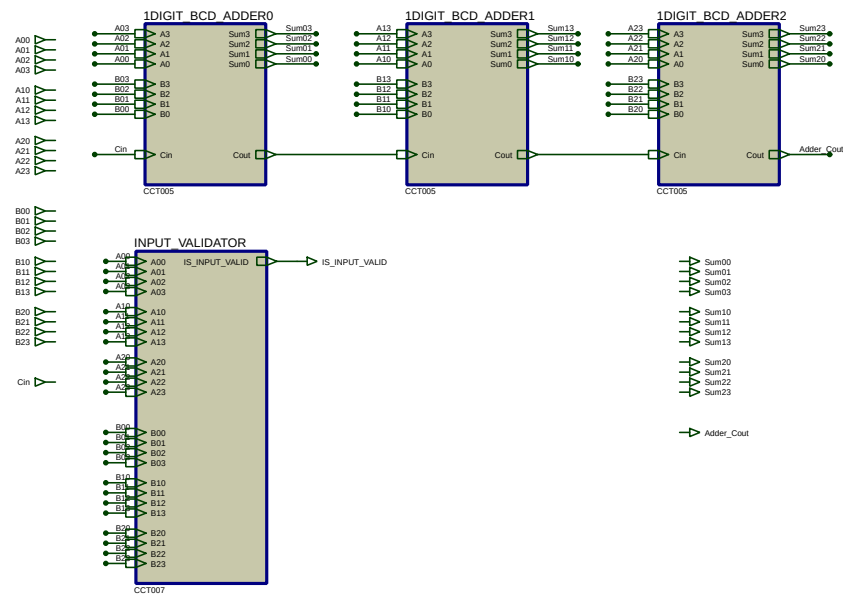


Figure 7: 3DIGIT_BCD_ADDER module.

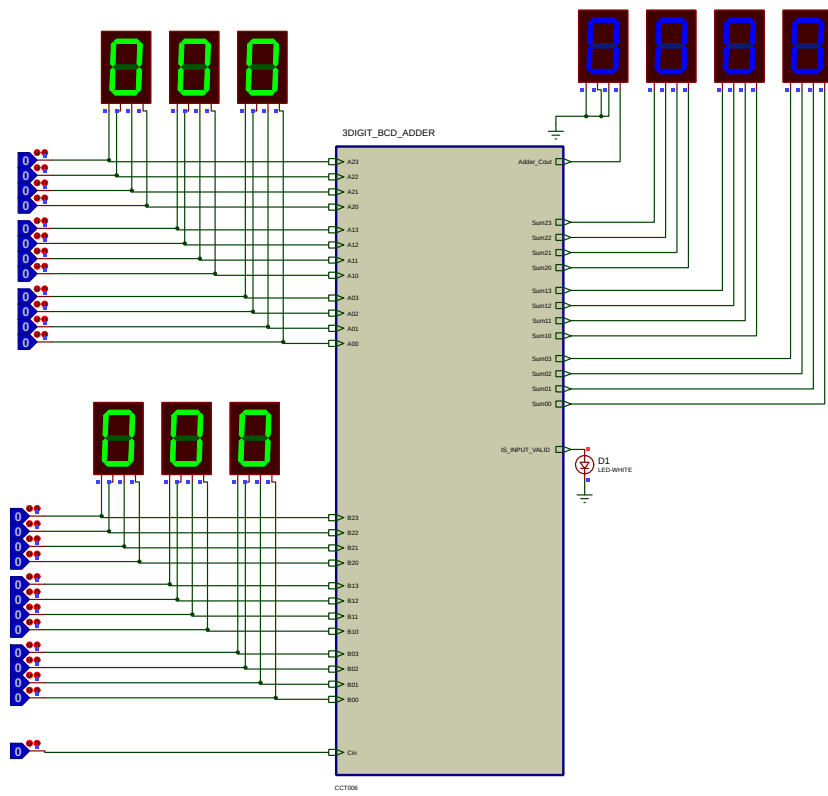


Figure 8: TOP module.

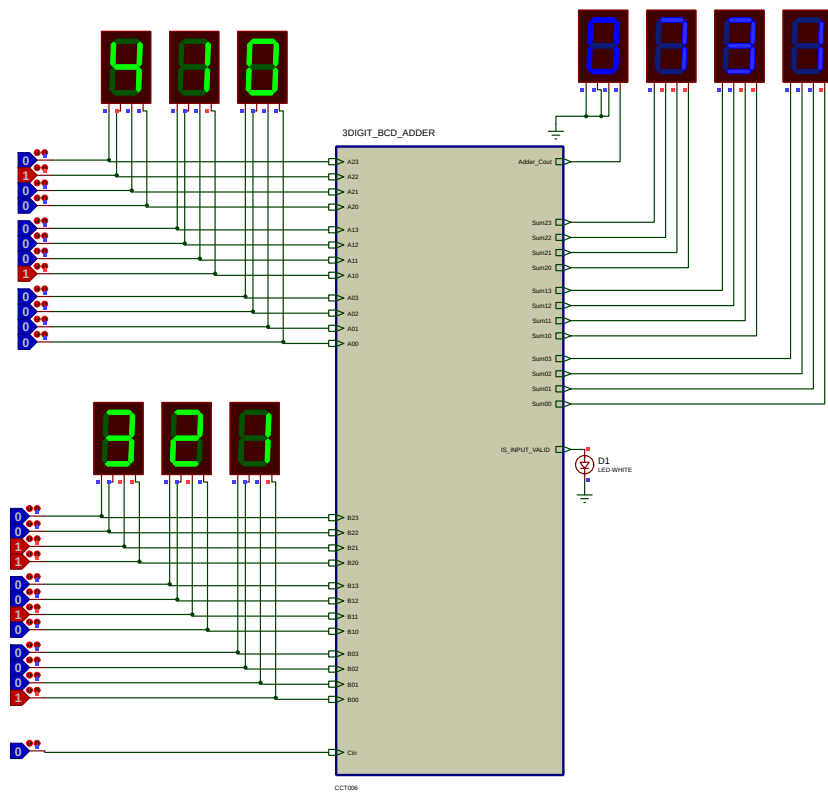


Figure 9: TOP module, performing a simple addition.

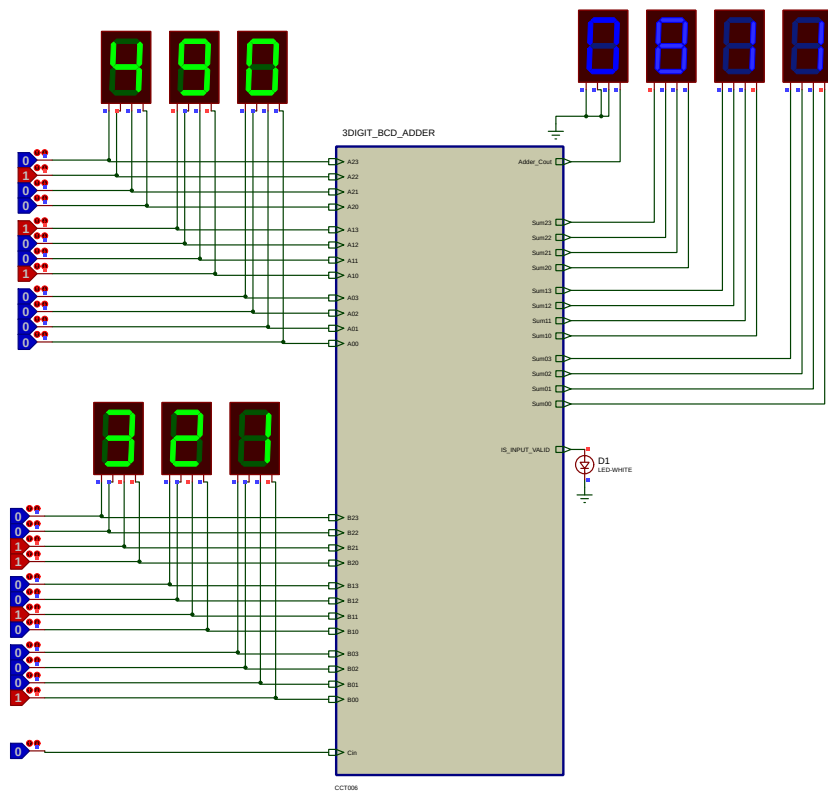


Figure 10: TOP module, performing an addition with a carry.

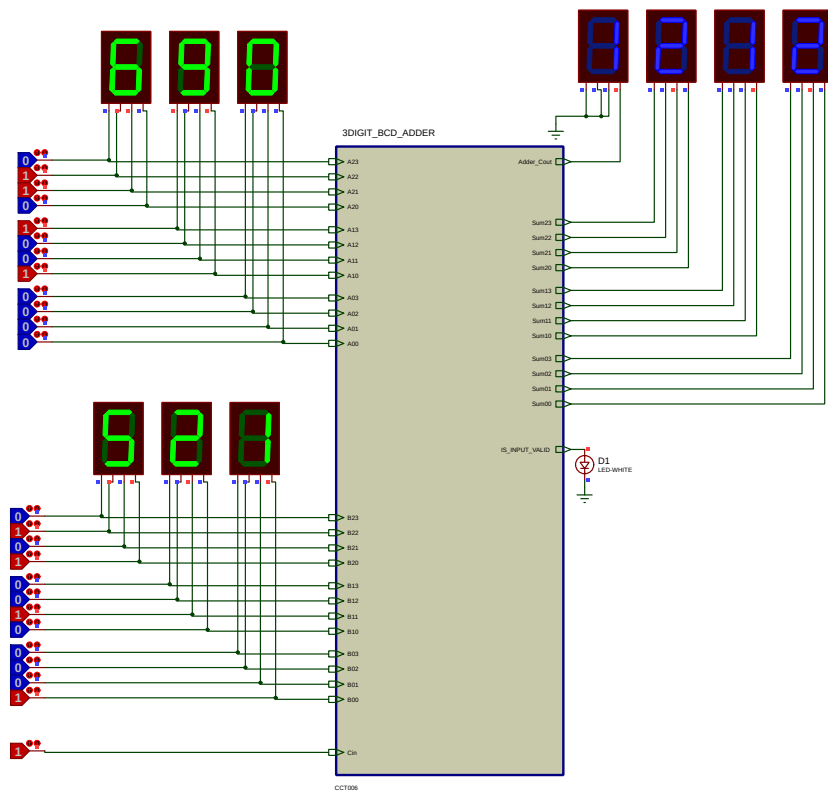


Figure 11: TOP module, performing an addition with all the carry bits enabled.

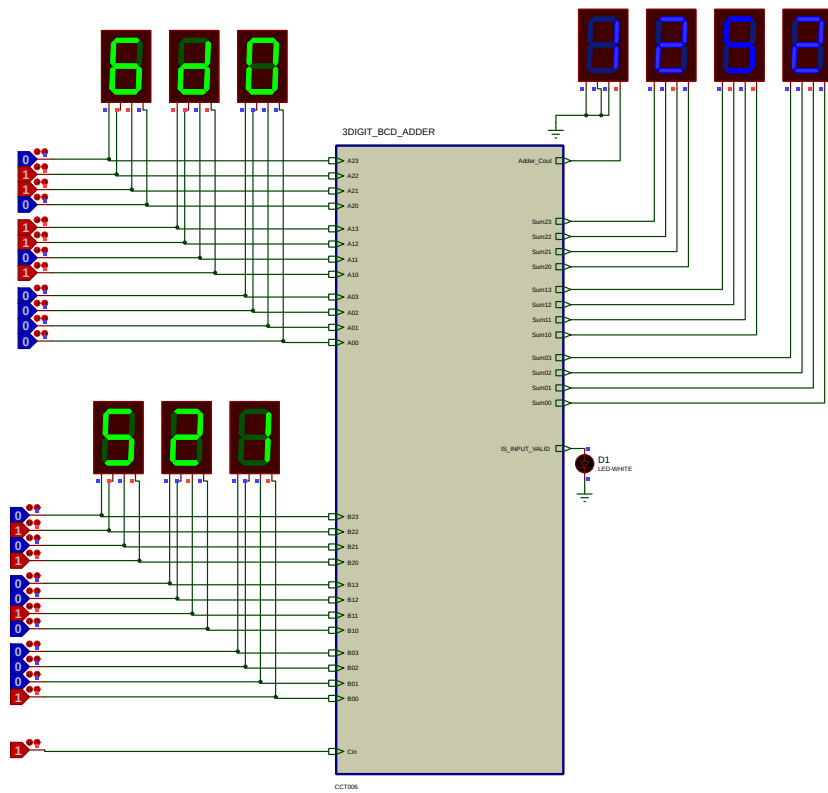


Figure 12: TOP module, setting IS_INPUT_VALID to 0 because one of the input digits is greater than 10.